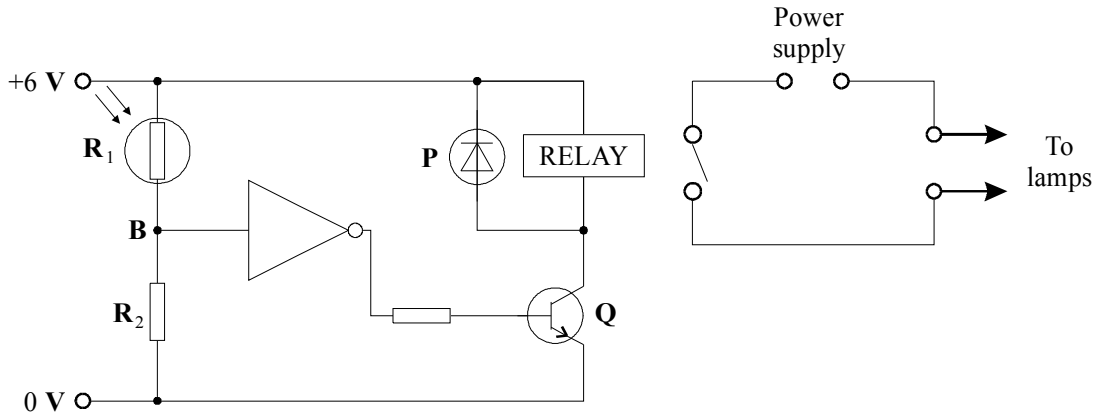


## Transistor Question

1 Figure 1 shows a circuit which can be used as an automatic switch.



**Figure 1**

(a) (i) Name component P.


.....

(ii) Why is component P included in the circuit?

.....

.....

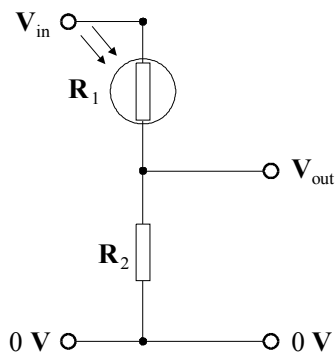Use the following information for part (b).



$$V_{\text{out}} = V_{\text{in}} \times \frac{R_2}{R_1 + R_2}$$

(b) The resistance of  $R_2 = 2000 \Omega$ .  
 $V_{\text{in}}$  is 6V.

(i) In daylight the resistance of  $R_1 = 5000 \Omega$ .  
 Calculate the voltage across  $R_2$ .

.....


.....

Voltage .....V

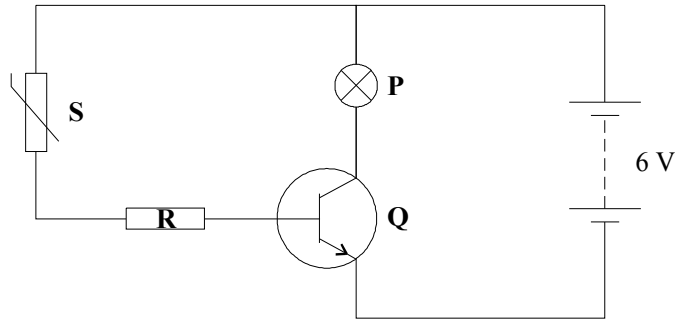(ii) In daylight the lamps will be OFF. Explain why.

.....  
.....  
.....  
.....  
.....  
.....

2 (a) The diagram shows a switching circuit. The lamp **P** switches on when the temperature reaches 5 °C.



(i) Which **one** of the following is the name of the component labelled **Q**? Underline your answer.

- diode      transformer      transistor

(ii) In the following sentence, cross out the two lines in the box that are wrong.

The resistor **R**


increases
does not affect
reduces

 the current going to component **Q**.

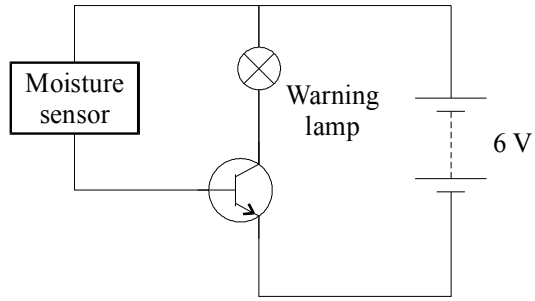(iii) Suggest **one** practical use for this circuit.

.....  
.....  
.....

- 3 (a) The diagram shows a simple moisture detector. The warning lamp lights when a current of 60 mA passes through it.



Someone with wet hands touches the moisture sensor. Explain why the warning lamp lights.

.....

.....


.....

.....

.....

.....

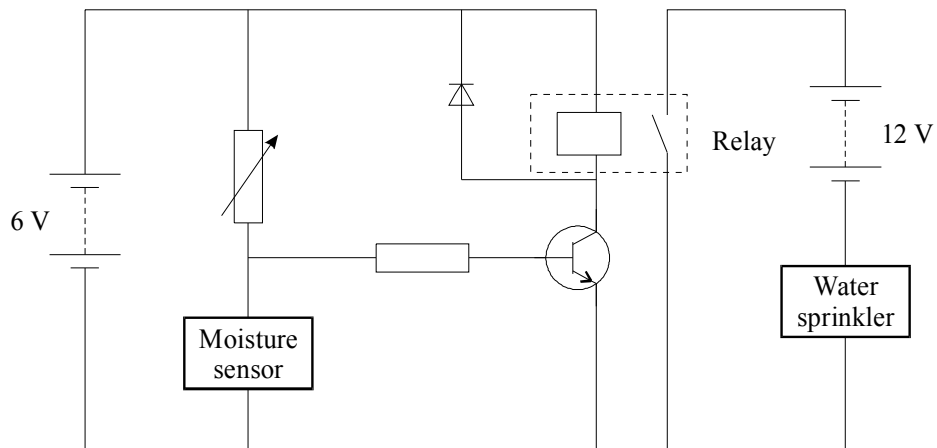- (b) The diagram shows a circuit designed to switch on a water sprinkler when the sensor detects very little moisture.



- (i) Why is a relay used to switch on the water sprinkler?

.....


.....

- (ii) How does changing the value of the variable resistor affect the circuit?

.....

.....

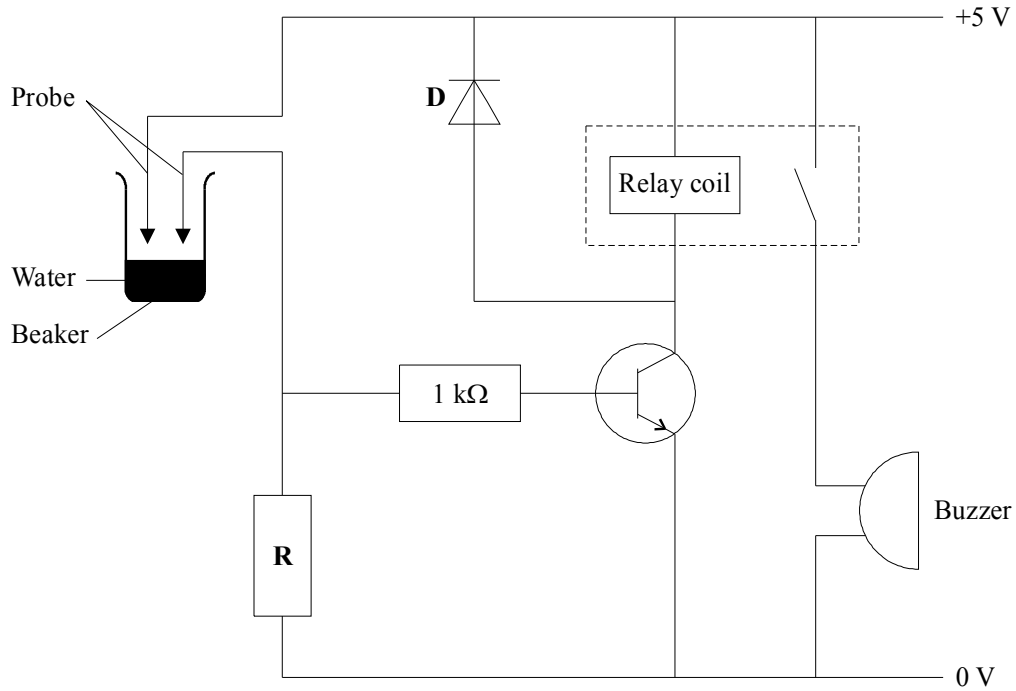4 (a) The circuit diagram shows one design for a moisture detector.



(i) In this circuit, what is the purpose of each of the  $1\text{ k}\Omega$  resistor;

.....  
 .....

(ii) When the water level in the beaker reaches the two metal probes the transistor switches and the buzzer sounds.

[A] Explain what happens to the circuit to cause the transistor to switch.

.....  
 .....  
 .....  
 .....

[B] Explain why, when the transistor switches, the buzzer sounds.

.....  
 .....  
 .....  
 .....

(iii) Suggest **one** practical use for this moisture detector.

